

PHYSICS

EXPERIMENT – 1

Aim: To determine resistance per cm of a given wire by plotting a graph of potential difference versus current.

Apparatus: A metallic conductor (coil or a resistance wire), a battery, one way key, a voltmeter and an ammeter of appropriate range, connecting wires and a piece of sand paper, a scale.

Formulae Used: The resistance (R) of the given wire (resistance coil) is obtained by Ohm's Law $\frac{V}{I} = R$

Where, V : Potential difference between the ends of the given resistance coil. (Conductor)

I: Current flowing through it.

If l is the length of resistance wire, then resistance per cm of the wire = $\frac{R}{l}$

Observation:

(i) Range:

Range of given voltmeter = 3 v

Range of given ammeter = 500 mA

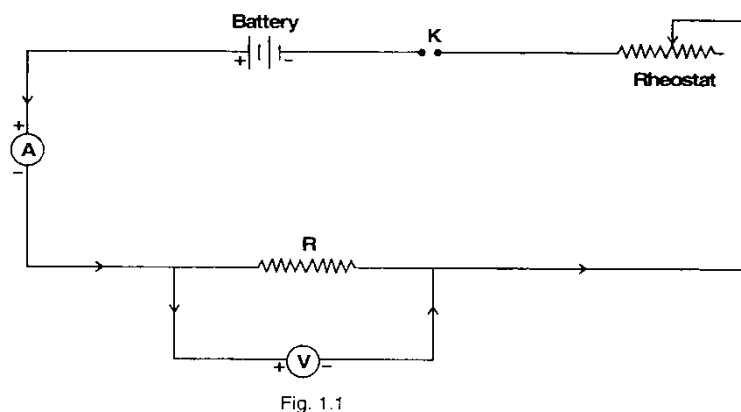


Fig. 1.1

(ii) Least count:

Least count of voltmeter = 0.05v

Least count of ammeter = 10 mA

(iii) Zero error:

Zero error in ammeter, $e_1 = 0$

Zero error in voltmeter, $e_2 = 0$

Ammeter and Voltmeter Readings:

Sr. No.	Ammeter Reading I (A)		Voltmeter Reading, V (v)		$\frac{V}{I} = R$
	Observed	Value	Observed	Value	
1	50	500 mA	16	$16 \times 0.05 = 0.8$	1.6Ω
2	35	350 mA	11	0.55	1.57Ω
3	32	320 mA	10	0.50	1.56Ω
4	19	190 mA	6	0.30	1.58Ω
5	10	100 mA	3	0.15	1.5Ω

Mean $R = 1.56$


Length of resistance wire: 28 cm

Graph between potential difference & current:

Scale: X – axis : 1 cm = 0.1 V of potential difference

Y – axis: 1 cm = 0.1 A of current

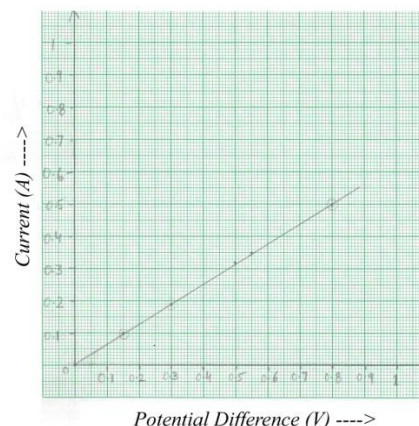The graph comes out to be a straight line.



Result: It is found that the ratio V/I is constant, hence current voltage relationship is established i.e. $V \propto I$ or Ohm's Law is verified.

Unknown resistance per cm of given wire = $5.57 \times 10^{-2} \Omega \text{ cm}^{-1}$

Precautions: Voltmeter and ammeter should be of proper range.

- The connections should be neat, clean & tight.

Source of Error: Rheostat may have high resistance.

The instrument screws may be loose.

EXPERIMENT – 2

Aim: To find resistance of a given wire using Whetstone's bridge (meter bridge) & hence determine the specific resistance of the material.

Apparatus: A meter bridge (slide Wire Bridge), a galvanometer, a resistance box, a laclanche cell, a jockey, a one-way key, a resistance wire, a screw gauge, meter scale, set square, connecting wires and sandpaper.

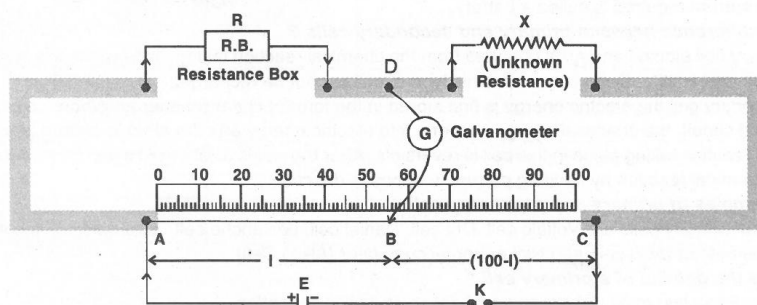


Fig. 2.1 Circuit Diagram - Meter Bridge

Formulae Used:

(i) The unknown resistance X is given by:

$$X = \frac{(100-l)}{l} \times R \quad \text{Where,}$$

R = known resistance placed in left gap.

X = Unknown resistance in right gap of meter bridge.

l = length of meter bridge wire from zero and upto balance point (in cm)

(ii) Specific resistance (ρ) of the material of given wire is given $\rho = \frac{X\pi D^2}{4L}$

Where,

D : Diameter of given wire

L : Length of given wire.

Observation Table for length (l) & unknown resistance, X :

Sr. No.	Resistance from resistance box R (ohm)	Length $AB = l$ cm	Length $BC = (100-l)$ cm	Unknown Resistance $X = R \cdot \frac{(100-l)}{l} \Omega$
1	2	41	59	2.87
2	4	60	40	2.66
3	6	69	31	2.69
4	8	76	24	2.52

Table for diameter (D) of the wire:

Sr. No.	Linear Scale Reading (N) mm	Circular Scale Reading		Observed diameter $D = N + n \times \text{L.C.}$ mm
		No. of circular scale divisions coinciding (n)	Value $n \times (\text{L.C.})$ mm	
1	0	34	0.34	0.34
2	0	35	0.35	0.35
3	0	36	0.36	0.36
4	0	35	0.35	0.35

Observations:

- Least count of screw gauge: 0.001 cm

Pitch of screw gauge: 0.1 cm

Total no. of divisions on circular scale: 100

$$\text{Least Count} = \frac{\text{Pitch}}{\text{No. of divisions on circular scale}}$$

$$\therefore LC = 0.001 \text{ cm}$$

- Length of given wire, $L = 25 \text{ cm}$

Calculation:

- For unknown resistance, X:

$$\text{Mean } X = \frac{X_1 + X_2 + X_3 + X_4}{4} = 2.68 \Omega$$

- Mean diameter, $D = \frac{D_1 + D_2 + D_3 + D_4}{4} = 0.035 \text{ cm}$

- Specific Resistance, $\rho = X \cdot \frac{\pi D^2}{4L} = 1.03 \times 10^{-4} \Omega \text{ cm}$

Result: Value of unknown resistance = 2.68Ω

Specific resistance of material of given wire = $1.03 \times 10^{-4} \Omega \text{ cm}$

Precautions: All plugs in resistance box should be tight. Plug in key, K should be inserted only while taking observations.

Sources of Error: Plugs may not be clean.

Instrument screws maybe loose.

EXPERIMENT – 3

Aim: To verify the laws of combination (series & parallel) of resistances using meter bridge (slide Wire Bridge)

Apparatus: A meter bridge, laclanche cell, a galvanometer, a resistance box, a jockey, two resistances wires, set square, sand paper and connecting wires.

(i) In series

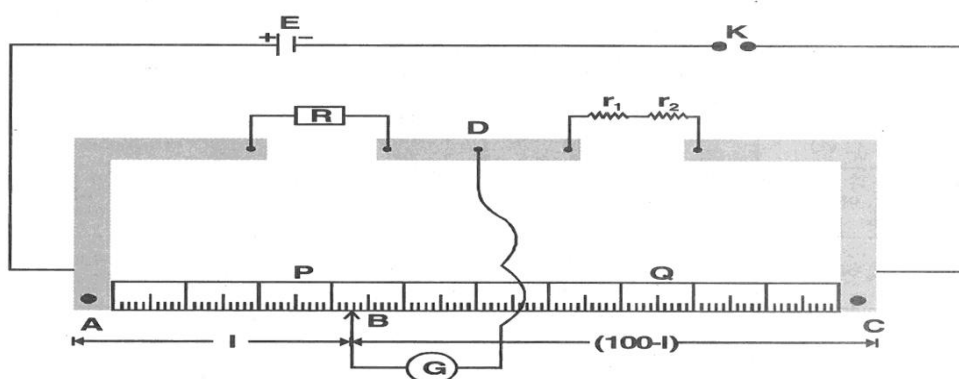


Fig. 3.1 Series combination of resistances

(ii) In parallel

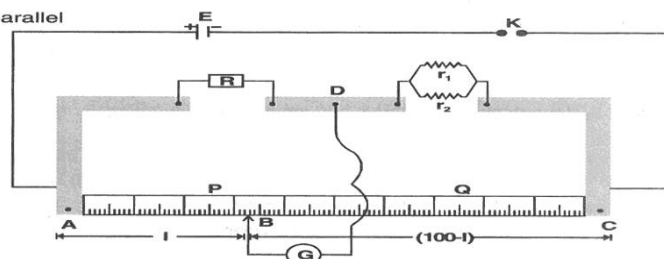


Fig. 3.2 Parallel combination of resistances

Observations: Table for length (l) & unknown resistance (r):